

Previous Courses

- Digital Devices (EE 3713/EE3714)
 - Boolean Algebra
 - Simple Combinational, Sequential Networks (< 50 gates)
 - TTL, PLD implementation technologies
 - No CAD tools
- Microprocessors
 - Instruction sets, basic architecture
 - Assembly language programming
 - Microprocessor based solutions for Digital control

BR 8/99

EE 4743/6743 : Digital Systems

- Complex Combinational and Sequential networks (up to thousands of gates)
 - Emphasis on combined datapath+Finite state machine designs for real time applications
- Modern CAD tool usage (schematic entry, simulation, technology mapping, timing analysis, synthesis)
- Logic Synthesis via VHDL
- Modern implementation technologies such Field Programmable Gate Arrays (FPGAs)

BR 8/99

Course Philosophy

- The textbook in this course is more of a reference
 - Buy it, READ IT. Will help, especially with logic synthesis
- Material in class based on instructor notes
 - Many notes online, see both:
www.ece.msstate.edu/~mitch/class/ee4743
www.ece.msstate.edu/~reese/EE4743
 - Course notes from previous semesters still applicable, but will be supplemented
- You will need to stay caught up on lecture material. Falling behind is difficult to recover from.

BR 8/99

Course Software

- We will use Altera Maxplus (runs on both PCs/Unix)
 - Runs great on any Pentium class machine that can run Win 98 (32 Mb RAM, 160 Mhz or better).
- Three student PC versions available (V 7.21, V 9.23, V10.1)
 - V9.23 is contained on the CDROM in the back of the textbook
 - Class WWW page has a link where you can download version V10.1 from the Altera WWW page.
 - Do not use V 7.21 – Use at least V9.23. Version 10.1 only needed if you are running Win2K or higher and want to download designs into the UP1 hardware board.
- Software also available on ECE Unix workstations also
 - See Class WWW page for instructions on using Maxplus on Unix workstations
 - Files are compatible between Unix workstation version and student versions.

BR 8/99

Course Software (cont)

Software is the same as used by practicing engineers in industry.

- **HIGHLY RECOMMEND** that you install it on your home PC
 - No competition for seats in lab
 - Eat popcorn, watch DVD, listen to music while you do homework
 - If you don't have a PC, *get one*. It is an indispensable tool for an engineer (plus, you can play some great games)

BR 8/99

Lecture, Labs

- Lecture is MW. Will meet on Fridays also for 'awhile' to get a fast start on material
 - Will get these 'extra' lectures back near end of semester when concentrating on project
- Only need to attend your lab session (Simrall workstation lab, 1st floor) to hear TA explanation of lab assignment
 - Can complete assignment on Unix machines or home PC. Upload files from home for TA checkoff.
- Lab assignments due ONE WEEK from your assigned lab time unless otherwise noted.

BR 8/99

Combinational Logic Review

Digital Devices was a **LONG, LONG** time ago in a galaxy **FAR, FAR, AWAY** for many of you.

We don't expect you to remember *everything* you learned in Digital Devices, but you need to remember > 0%.

We will review some to help you remember. You also need to go back and look at old notes. After a couple of days of review, we will expect you to be up to speed, and then we will **zoom** along.


Ask QUESTIONS during CLASS to SLOW things down.

BR 8/99

7404 Logic Gate

Mixed Logic

A	Y
L	H
H	L

 


Buffer that converts high true input to low true output

A	Y (L)
0	0
1	1

Fixed Logic

A	Y
0	1
1	0

 


Buffer that converts low true input to high true output

A(L)	Y
1	1
0	0

BR 8/99

A	B	Y
L	L	L
L	H	L
H	L	L
H	H	L

7408

 


AND



A	B	Y
L	L	L
L	H	H
H	L	H
H	H	H

7432

 


OR



A	B	Y
L	L	H
L	H	H
H	L	H
H	H	L

7400

 

NAND




A	B	Y
L	L	H
L	H	L
H	L	L
H	H	L

7402




NOR

 

Gate Summaries


BR 8/99

Majority Gate (and-or) form

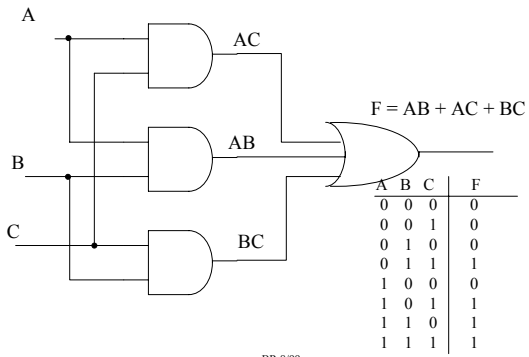


BR 8/99

Majority Gate (nand-nand) form

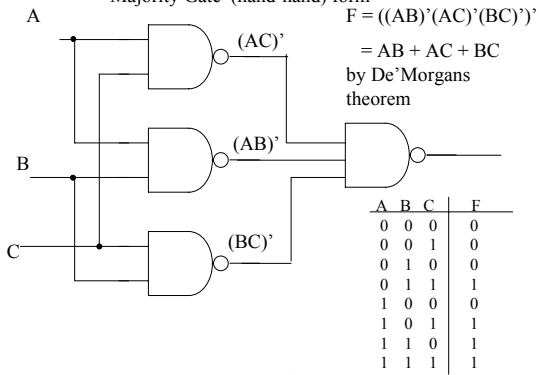

BR 8/99

Majority Gate (mixed logic) form

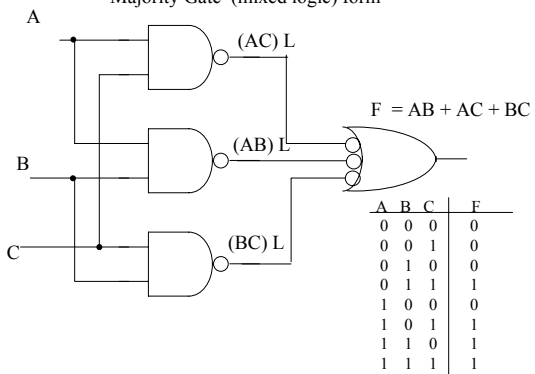

BR 8/99

Boolean Minimization

Reduce a boolean equation to fewer terms - hopefully, this will result in using less gates to implement the boolean equation.

Pencil-Paper: Algebraic techniques, K-maps

Automated: Many powerful algorithms exist

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$F = A'BC + AB'C + ABC' + ABC$$

$$F = BC + AC + AB$$

Find Boolean adjacencies to minimize equation; eliminate redundant term

BR 8/99

K- maps

Graphical Aid for minimization - used to visualize boolean adjacencies

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

A \ BC	00	01	11	10
	0	0	1	0
1	0	1	1	1

A \ BC	00	01	11	10
	0	0	1	0
1	0	1	1	1

$$F = BC + AC + AB$$

BR 8/99

Technology Mapping

Technology mapping is takes a boolean equation and maps it onto a given technology. The technology can affect what constraints are used when doing minimization for the function.




Discrete gates

Programmable Logic


Custom Integrated Circuits

BR 8/99

$$F = AB + BC + AC$$

   

Lookup Table

 

BR 8/99

Logic Synthesis

Logic Synthesis: convert a description of a digital system in a Hardware Description Language (HDL) to an implementation technology.

HDL description

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity majority is
  port ( A, B, C : in std_logic;
        Y: out std_logic
  );
end majority;
```

ARCHITECTURE a of majority is

begin

```
Y <= (A and B) or (A and C) or (B and C);
end a;
```

Synthesis



Gates



BR 8/99

Combinational Building Blocks


1 bit Multiplexor (MUX)

  

Muxes often use to select groups of bits arranged in busses.

BR 8/99

Decoder

 

BR 8/99

Memories

Memories are classified as $K \times N$ devices, K is the # of locations, N is the number bits per location (16 x 2 would be 16 locations, each storing 2 bits)

K locations require $\log_2(K)$ address lines for selecting a location (i.e. a 16 location memory needs 4 address lines)

A memory that is $K \times N$, can be used to implement N boolean equations, which use $\log_2(K)$ variables (the N boolean equations must use the same variables).

One address line is used for each boolean variable, each bit of the output implements a different boolean equation.

The memory functions as a *LookUp Table (LUT)*.

BR 8/99

Memory example

$$F(A,B,C) = A \text{ xor } B \text{ xor } C \quad G = AB + AC + BC$$

A	B	C	F	G
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Recall that Exclusive OR (xor) is

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

$$Y = A \oplus B \\ = A \text{ xor } B$$



BR 8/99

 

LookUp Table (LUT)


$A[2:0]$ is 3 bit address bus, $D[1:0]$ is 2 bit output bus.

Location 0 has "00",
Location 1 has "10",
Location 2 has "10",
etc....

Binary Adder



$$F(A,B,C) = A \text{ xor } B \text{ xor } C \quad G = AB + AC + BC$$

 These equations look familiar. Recall what a **Full Adder** is:




BR 8/99

4 Bit Ripple Carry Adder

  


BR 8/99

Propagation Delay

 

BR 8/99

Propagation Delay (non inverting)

 

Making a Design Run Fast

- Speed usually much more important than saving gates.
- The speed of a gate directly affects the maximum clock speed of digital system
- Gate speed is TECHNOLOGY dependent
 - 0.35u CMOS process has faster gates than 0.8u CMOS process
- Implementation choice will affect Design speed
 - A Custom integrated circuit will be faster than an FPGA implementation.
- Design approaches will affect clock speed of system
 - Smart designers can make a big difference

BR 8/99

Summary

- Need to review your Digital Devices notes
 - Basic Gates, Boolean algebra (algebraic minimization, up to four variable K-maps), Combinational building blocks (muxes, decoders, memories, adders)
- We will discuss Hardware Description Languages
 - VHDL is the language used in the class
- We will discuss modern implementation technologies, primarily Field Programmable Gate Arrays (FPGAs)
- We will discuss design strategies for making designs run faster, not necessarily take less gates.

BR 8/99
