

Concurrent Signal Assignment Statements

Outline

1. Combinational versus sequential circuit
2. Simple signal assignment statement
3. Conditional signal assignment statement
4. Selected signal assignment statement
5. Conditional vs. selected signal assignment

RTL Hardware Design

Chapter 4

1

RTL Hardware Design

Chapter 4

2

1. Combinational vs. sequential circuit

- Combinational circuit:
 - No internal state
 - Output is a function of inputs only
 - No latches/FFs or closed feedback loop
- Sequential circuit:
 - With internal state
 - Output is a function of inputs and internal state
- Sequential circuit to be discussed later

RTL Hardware Design

Chapter 4

3

2. Simple signal assignment statement

- Simple signal assignment is a special case of conditional signal assignment
- Syntax:
`signal_name <= projected_waveform;`
- E.g.,
`y <= a + b + 1 after 10 ns;`
- Timing info ignored in synthesis and δ -delay is used:
`signal_name <= value_expression`

RTL Hardware Design

Chapter 4


5

RTL Hardware Design

Chapter 4

4

 - E.g.,
`status <= '1';`
`even <= (p1 and p2) or (p3 and p4);`
`arith_out <= a + b + c - 1;`
- Implementation of last statement



RTL Hardware Design

Chapter 4

6

Signal assignment statement with a closed feedback loop

- a signal appears in both sides of a concurrent assignment statement
- E.g.,
q <= ((not q) and (not en)) or (d and en);
- Syntactically correct
- Form a closed feedback loop
- Should be avoided

3. Conditional signal assignment statement

- Syntax
- Examples
- Conceptual implementation
- Detailed implementation examples

Syntax

- Simplified syntax:

```
signal_name
  <= value_expr_1 when boolean_expr_1 else
    value_expr_2 when boolean_expr_2 else
    value_expr_3 when boolean_expr_3 else
    ...
    value_expr_n
```

E.g., 4-to-1 mux

- Function table:

input	output
s	x
0 0	a
0 1	b
1 0	c
1 1	d

```
library ieee;
use ieee.std_logic_1164.all;
entity mux4 is
  port(
    a,b,c,d: in std_logic_vector(7 downto 0);
    s: in std_logic_vector(1 downto 0);
    x: out std_logic_vector(7 downto 0)
  );
end mux4 ;
architecture cond_arch of mux4 is
begin
  x <= a when (s="00") else
    b when (s="01") else
    c when (s="10") else
    d;
end cond_arch;
```

E.g., 2-to-2² binary decoder

- Function table:

input	output
s	x
0 0	0001
0 1	0010
1 0	0100
1 1	1000

```

library ieee;
use ieee.std_logic_1164.all;
entity decoder4 is
    port(
        s: in  std_logic_vector(1 downto 0);
        x: out std_logic_vector(3 downto 0)
    );
end decoder4 ;
architecture cond_arch of decoder4 is
begin
    x <= "0001" when (s="00") else
        "0010" when (s="01") else
        "0100" when (s="10") else
        "1000";
end cond_arch;

```

RTL Hardware Design

Chapter 4

13

E.g., 4-to-2 priority encoder

- Function table:

input r	output	
	code	active
1---	11	1
01--	10	1
001-	01	1
0001	00	1
0000	00	0

- Function table:

input ctrl	output	
	code	active
0--	src0 + 1	
100	src0 + src1	
101	src0 - src1	
110	src0 and src1	
111	src0 or src1	

```

library ieee;
use ieee.std_logic_1164.all;
entity prio_encoder42 is
    port(
        r: in  std_logic_vector(3 downto 0);
        code: out std_logic_vector(1 downto 0);
        active: out std_logic
    );
end prio_encoder42;
architecture cond_arch of prio_encoder42 is
begin
    code <= "11" when (r(3)='1') else
        "10" when (r(2)='1') else
        "01" when (r(1)='1') else
        "00";
    active <= r(3) or r(2) or r(1) or r(0);
end cond_arch ;

```

RTL Hardware Design

Chapter 4

15

RTL Hardware Design

Chapter 4

16

E.g., simple ALU

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity simple_alu is
    port(
        ctrl: in  std_logic_vector(2 downto 0);
        src0, src1: in std_logic_vector(7 downto 0);
        result: out std_logic_vector(7 downto 0)
    );
end simple_alu ;
architecture cond_arch of simple_alu is
    signal sum, diff, inc: std_logic_vector(7 downto 0);
begin
    inc <= std_logic_vector(signed(src0)+1);
    sum <= std_logic_vector(signed(src0)+signed(src1));
    diff <= std_logic_vector(signed(src0)-signed(src1));
    result <= inc when ctrl(2)='0' else
        sum when ctrl(1 downto 0)="00" else
        diff when ctrl(1 downto 0)="01" else
        src0 and src1 when ctrl(1 downto 0)="10" else
        src0 or src1;
end cond_arch;

```

RTL Hardware Design

Chapter 4

17

RTL Hardware Design

Chapter 4

18

Conceptual implementation


- Syntax:


```

signal_name
    <= value_expr_1 when boolean_expr_1 else
        value_expr_2 when boolean_expr_2 else
        value_expr_3 when boolean_expr_3 else
        ...
        value_expr_n;
            
```
- Evaluation in ascending order
- Achieved by “priority-routing network”
- Top value expression has a “higher priority”

2-to-1 “abstract” mux

 - sel has a data type of boolean
- If sel is true, the input from “T” port is connected to output.
- If sel is false, the input from “F” port is connected to output.




RTL Hardware Design

Chapter 4

19
 
```
signal_name <= value_expr_1 when boolean_expr_1 else
               value_expr_2;
```




RTL Hardware Design

Chapter 4

20

 
```
signal_name <= value_expr_1 when boolean_expr_1 else
               value_expr_2 when boolean_expr_2 else
               value_expr_3 when boolean_expr_3 else
               value_expr_4;
```



RTL Hardware Design

Chapter 4

21

 


RTL Hardware Design

Chapter 4

22

Detailed implementation examples

- 2-to-1 mux

 


RTL Hardware Design

Chapter 4

23

- E.g.,
 
```
signal a,b,y: std_logic;
y <= '0' when a=b else
    '1';
```



RTL Hardware Design

Chapter 4



24

- E.g.,

```

signal a,b,c,x,y,r: std_logic;
...
r <= a when x=y else
    b when x>y else
    c;

```

  


- E.g.,

```

...
signal a,b,r: unsigned(7 downto 0);
signal x,y: unsigned(3 downto 0);
...
r <= a+b when x+y>1 else
    a-b-1 when x>y and y!=0 else
    a+1;

```

 

4. Selected signal assignment statement

- Syntax
- Examples
- Conceptual implementation
- Detailed implementation examples

Syntax

- Simplified syntax:

```

with select_expression select
signal_name <=
    value_expr_1 when choice_1,
    value_expr_2 when choice_2,
    value_expr_3 when choice_3,
    ...
    value_expr_n when choice_n;

```

- select_expression
 - Discrete type or 1-D array
 - With finite possible values
- choice_i
 - A value of the data type
- Choices must be
 - mutually exclusive
 - all inclusive
 - **others** can be used as last choice_i

E.g., 4-to-1 mux

```
architecture sel_arch of mux4 is
begin
  with s select
    x <= a when "00",
         b when "01",
         c when "10",
         d when others;
end sel_arch ;
```

input s	output x
00	a
01	b
10	c
11	d

RTL Hardware Design

Chapter 4

31

- Can "11" be used to replace **others**?

```
with s select
  x <= a when "00",
       b when "01",
       c when "10",
       d when "11";
```

RTL Hardware Design

Chapter 4

32

E.g., 2-to-2² binary decoder

```
architecture sel_arch of decoder4 is
begin
  with sel select
    x <= "0001" when "00",
         "0010" when "01",
         "0100" when "10",
         "1000" when others;
end sel_arch ;
```

input s	output x
00	0001
01	0010
10	0100
11	1000

RTL Hardware Design

Chapter 4

33

E.g., 4-to-2 priority encoder

```
architecture sel_arch of prio_encoder42 is
begin
  with r select
    code <= "11" when "1000"|"1001"|"1010"|"1011"|"1100"|"1101"|"1110"|"1111",
             "10" when "0100"|"0101"|"0110"|"0111",
             "01" when "0010"|"0011",
             "00" when others;
    active <= r(3) or r(2) or r(1) or r(0);
end sel_arch;
```

input r	code	active
1---	11	1
01--	10	1
001-	01	1
0001	00	1
0000	00	0

RTL Hardware Design

Chapter 4

E.g., simple ALU

- Can we use '-'?

```
with a select
  x <= "11" when "1---",
       "10" when "01--",
       "01" when "001-",
       "00" when others;
```

```
architecture sel_arch of simple_alu is
  signal sum, diff, inc: std_logic_vector(7 downto 0);
begin
  inc <= std_logic_vector(signed(src0)+1);
  sum <= std_logic_vector(signed(src0)+signed(src1));
  diff <= std_logic_vector(signed(src0)-signed(src1));
  with ctrl select
    result <= inc when "000"|"001"|"010"|"011",
              sum  when "100",
              diff  when "101",
              src0 and src1 when "110",
              src0 or src1  when others;
end sel_arch;
```

input ctrl	output result
0--	src0 + 1
100	src0 + src1
101	src0 - src1
110	src0 and src1
111	src0 or src1

RTL Hardware Design

Chapter 4

35

RTL Hardware Design

Chapter 4

E.g., Truth table

```

library ieee;
use ieee.std_logic_1164.all;
entity truth_table is
    port(
        a,b: in  std_logic;
        y: out std_logic
    );
end truth_table;
architecture a of truth_table is
    signal tmp: std_logic_vector(1 downto 0);
begin
    tmp <= a & b;
    with tmp select
        y <= '0' when "00",
            '1' when "01",
            '1' when "10",
            '1' when others; -- "11"
end a;

```

RTL Hardware Design


Chapter 4

37

input	output
ab	y
00	0
01	1
10	1
11	1

Conceptual implementation

 - Achieved by a multiplexing circuit
- Abstract (k+1)-to-1 multiplexer
 - sel is with a data type of (k+1) values: c0, c1, c2, . . . , ck



RTL Hardware Design

Chapter 4


38

- select_expression is with a data type of 5 values: c0, c1, c2, c3, c4

```

with select_expression select
    sig <= value_expr_0 when c0,
        value_expr_1 when c1,
        value_expr_n when others;

```

 

RTL Hardware Design

Chapter 4

39


RTL Hardware Design

Chapter 4

40

Detailed implementation examples

- 4-to-1 mux

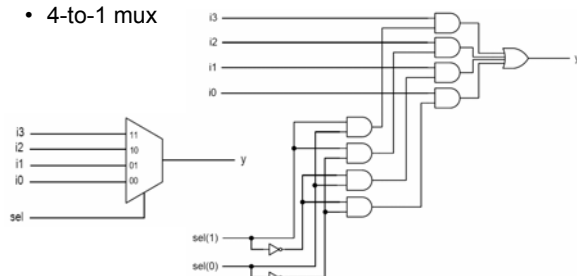

RTL Hardware Design

Chapter 4

41


- E.g.,


```

signal a,b,r: unsigned(7 downto 0);
signal s: std_logic_vector(1 downto 0);

with s select
    r <= a+1 when "11",
        a-b-1 when "10",
        a+b when others;

```

 

RTL Hardware Design

Chapter 4

42

3. Conditional vs. selected signal assignment

- Conversion between conditional vs. selected signal assignment
- Comparison

RTL Hardware Design

Chapter 4

43

From selected assignment to conditional assignment

```
with sel select
  sig <= value_expr_0 when c0,
         value_expr_1 when c1|c3|c5,
         value_expr_2 when c2|c4,
         value_expr_n when others;

sig <=
  value_expr_0 when (sel=c0) else
  value_expr_1 when (sel=c1) or (sel=c3) or (sel=c5) else
  value_expr_2 when (sel=c2) or (sel=c4) else
  value_expr_n;
```

RTL Hardware Design

Chapter 4

44

From conditional assignment to selected assignment

```
sig <= value_expr_0 when bool_exp_0 else
      value_expr_1 when bool_exp_1 else
      value_expr_2 when bool_exp_2 else
      value_expr_n;

sel(2) <= '1' when bool_exp_0 else '0';
sel(1) <= '1' when bool_exp_1 else '0';
sel(0) <= '1' when bool_exp_2 else '0';
with sel select
  sig <= value_expr_0 when "100"|"101"|"110"|"111",
         value_expr_1 when "010"|"011",
         value_expr_2 when "001",
         value_expr_n when others;
```

RTL Hardware Design

Chapter 4

45

Comparison

- Selected signal assignment:
 - good match for a circuit described by a functional table
 - E.g., binary decoder, multiplexer
 - Less effective when an input pattern is given a preferential treatment

RTL Hardware Design

Chapter 4

46

- Conditional signal assignment:
 - good match for a circuit a circuit that needs to give preferential treatment for certain conditions or to prioritize the operations
 - E.g., priority encoder
 - Can handle complicated conditions. e.g.,

```
pc_next <=
  pc_reg + offset when (state=jump and a=b) else
  pc_reg + 1 when (state=skip and flag='1') else
  . . .
```

RTL Hardware Design

Chapter 4

47

- May “over-specify” for a functional table based circuit.

```
– E.g., mux  x <= a when (s="00") else
              b when (s="01") else
              c when (s="10") else
              d;
```

```
x <= c when (s="10") else
     a when (s="00") else
     b when (s="01") else
     d;
```

```
x <= c when (s="10") else
     b when (s="01") else
     a when (s="00") else
     d;
```

RTL Hardware Design

Chapter 4

48