

## Clock and Synchronization

## Outline

1. Why synchronous?
2. Clock distribution network and skew
3. Multiple-clock system
4. Meta-stability and synchronization failure
5. Synchronizer

## 1. Why synchronous



## Timing of a combinational digital system

- Steady state
  - Signal reaches a stable value
  - Modeled by Boolean algebra
- Transient period
  - Signal may fluctuate
  - No simple model
- Propagation delay: time to reach the steady state

  
## Timing Hazards

- Hazards: the fluctuation occurring during the transient period
  - Static hazard: glitch when the signal should be stable
  - Dynamic hazard: a glitch in transition
- Due to the multiple converging paths of an output port


- E.g., static-hazard ( $sh = ab' + bc$ ;  $a=c=1$ )



- E.g., dynamic hazard ( $a=c=d=1$ )

 

(a) Schematic

 

(b) Timing diagram

RTL Hardware Design  
by P. Chu

7

E.g., Hazard of circuit with closed feedback loop (async seq circuit)





c	q*
0	q
1	d

(a) D latch

```
library ieee;
use ieee.std_logic_1164.all;
entity dlatch is
    port(
        c: in std_logic;
        d: in std_logic;
        q: out std_logic
    );
end dlatch;
architecture demo_arch of dlatch is
    signal q_latch: std_logic;
begin
    process (c, d, q_latch)
    begin
        if (c='1') then
            q_latch <= d;
        else
            q_latch <= q_latch;
        end if;
        q <= q_latch;
    end process;
end demo_arch;
```

RTL Hardware Design  
by P. Chu

  


RTL Hardware Design  
by P. Chu

9
 
## Dealing with hazards

- In a small number of cases, additional logic can be added to eliminate race (and hazards).



(c) Revised Karnaugh map and schematic to eliminate hazards

RTL Hardware Design  
by P. Chu

Chapter 16

10


- This is not feasible for synthesis
- What's can go wrong:
  - During logic synthesis, the logic expressions will be rearranged and optimized.
  - During technology mapping, generic gates will be re-mapped
  - During placement & routing, wire delays may change
  - It is bad for testing verification

RTL Hardware Design  
by P. Chu


Chapter 16

11

 - Better way to handle hazards
  - Ignore glitches in the transient period and retrieve the data after the signal is stabilized
- In a sequential circuit
  - Use a clock signal to sample the signal and store the stable value in a register.
  - But register introduces new timing constraint (setup time and hold time)



 - Synchronous system:
  - group registers into a single group and drive them with the same clock
  - Timing analysis for a single feedback loop



RTL Hardware Design  
by P. Chu

Chapter 16

13

## Synchronous circuit and EDA

- Synthesis: reduce to combinational circuit synthesis
- Timing analysis: involve only a single closed feedback loop (others reduce to combinational circuit analysis)
- Simulation: support “cycle-based simulation”
- Testing: can facilitate scan-chain

RTL Hardware Design  
by P. Chu

Chapter 16

14

## 2. Clock distribution network and skew

### Clock distribution network

- Ideal clock: clock's rising edges arrive at FFs at the same time
- Real implementation:
  - Driving capability of each cell is limited
  - Need a network of buffers to drive all FFs
  - In ASIC: done by clock synthesis (a step in physical synthesis)
  - In FPGA: pre-fabricated clock distribution network

RTL Hardware Design  
by P. Chu

Chapter 16


15

RTL Hardware Design  
by P. Chu

Chapter 16

16

- Block diagram

 


RTL Hardware Design  
by P. Chu

Chapter 16


17

- Ideal H-routing

 
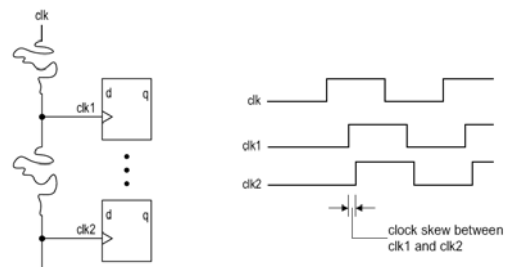
### Clock skew

- Skew: time difference between two arriving clock edges





RTL Hardware Design  
by P. Chu

Chapter 16

18

  - Setup time constraint (impact on max clock rate)
- Hold time constraint




$$\begin{aligned} t_3 &< t_4 \\ t_3 &= t_0 + T_{cq} + T_{next(max)} \\ t_4 &= t_3 - T_{setup} = (t_0 + T_c + T_{skew}) - T_{setup} \\ T_{cq} + T_{next(max)} + T_{setup} - T_{skew} &< T_c \\ T_{c(min)} &= T_{cq} + T_{next(max)} + T_{setup} - T_{skew} \end{aligned}$$

- Clock skew actually helps increasing clock rate in this particular case

- If the clock signal travels from the opposite direction

$$T_{c(min)} = T_{cq} + T_{next(max)} + T_{setup} + T_{skew}$$

 - Normally we have to consider the worst case since
  - No control on clock routing during synthesis
  - Multiple feedback paths



- Hold time constraint

$$\begin{aligned} t_h &< t_2 \\ t_2 &= t_0 + T_{cq} + T_{next(min)} \\ t_h &= t_0 + T_{hold} + T_{skew} \\ T_{hold} &< T_{ca} + T_{next(min)} - T_{skew} \\ T_{hold} &< T_{cq} - T_{skew} \end{aligned}$$

- Skew may reduce hold time margin
- Hold time violation cannot be corrected in RT level

- Summary

- Clock skew normally has negative impact on synchronous sequential circuit
- Effect on setup time constraint: require to increase clock period (i.e., reduce clock rate)
- Effect on hold time constraint: may introduce hold time violation
  - Can only be fixed during physical synthesis: re-route clock; re-place register and comb logic; add artificial delay logic
- Skew within 10% of clock period tolerable

### 3. Multiple-clock system

### Why multiple clocks

- Inherent multiple clock sources
  - E.g., external communication link
- Circuit size
  - Clock skew increases with the # FFs in a system
  - Current technology can support up to  $10^4$  FFs
- Design complexity
  - E.g., as system w/ 16-bit 20 MHz processor, 1-bit 100 MHz serial interface, 1 MHz I/O controller
- Power consideration
  - Dynamic power proportional to switching freq

### Derived vs Independent clocks

- Independent clocks:
  - Relationship between the clocks is unknown
- Derived clocks:
  - A clock is derived from another clock signals (e.g., different clock rate or phase)
  - Relationship is known
  - Logic for the derived clock should be separated from regular logic and manually synthesized (e.g., special delay line or PLL)
  - A system with derived clock can still be treated and analyzed as a synchronous system


### GALS

- Globally asynchronous locally synchronous system
  - Partition a system into multiple clock domains
  - Design and verify subsystem in same clock domain as a synchronous system
  - Design special interface between clock domains

### 4. Meta-stability and synchronization failure
 
### Timing analysis of a synchronous system

- To satisfy setup time constraint:
  - Signal from the state register
    - Controlled by clock
    - Adjust clock period to avoid setup time violation
  - Signal from external input
    - Same if the external input comes from another synchronous subsystem
    - Otherwise, have to deal with the occurrence of setup time violation.




RTL Hardware Design  
by P. Chu

Chapter 16

31

## Metastability

- What happens after timing violation?

 

RTL Hardware Design  
by P. Chu

Chapter 16

32

- Output of FF becomes 1 (sampled old input value)
- Output of FF becomes 0 (sampled new input value)
- FF enters metastable state, the output exhibits an “in-between” value
  - FF eventually “resolves” to one of stable states
  - The resolution time is a random variable with distribution function ( $\tau$  is decay constant)

$$P(T_r) = e^{-\frac{T_r}{\tau}}$$

- The probability that metastability persists beyond  $T_r$  (i.e., cannot be resolved within  $T_r$ )

## MTBF( $T_r$ )

- Synchronization failure
  - an FF cannot resolve the metastable condition within the given time
- MTBF
  - Mean Time Between synchronization Failures
  - Basic criterion for metastability analysis
  - Frequently expressed as a function of  $T_r$  (resolution time provided)

RTL Hardware Design  
by P. Chu

Chapter 16

33

RTL Hardware Design  
by P. Chu

Chapter 16

34

### • MTBF computation

- $R_{meta}$ : The average rate at which an FF enters the metastable state.
- $P(T_r)$ : The probability that an FF cannot resolve the metastable condition within  $T_r$ .

$$R_{meta} = w * f_{clk} * f_d$$

$w$  is the susceptible time window

$$P(T_r) = e^{-\frac{T_r}{\tau}}$$

$$AF(T_r) = R_{meta} * P(T_r) = w * f_{clk} * f_d * e^{-\frac{T_r}{\tau}}$$

$$MTBF(T_r) = \frac{1}{AF(T_r)} = \frac{e^{\frac{T_r}{\tau}}}{w * f_{clk} * f_d}$$

RTL Hardware Design  
by P. Chu

Chapter 16

35

- E.g.,  $w=0.1\text{ns}$ ,  $\tau=0.5\text{ns}$ ,  $f_{clk}=50\text{MHz}$ ,  $f_d=0.1f_{clk}$

$T_r$	MTBF
0.0 ns	$4.00 * 10^{-05}$ sec (0.04 msec)
2.5 ns	$5.94 * 10^{-03}$ sec (5.94 msec)
5.0 ns	$8.81 * 10^{-01}$ sec (0.88 sec)
7.5 ns	$1.31 * 10^{+02}$ sec (131 sec)
10.0 ns	$1.94 * 10^{+04}$ sec (5.39 hours)
12.5 ns	$2.88 * 10^{+06}$ sec (3.33 days)
15.0 ns	$4.27 * 10^{+08}$ sec (1.36 years)
17.5 ns	$6.34 * 10^{+10}$ sec ( $2.01 * 10^3$ years)
20.0 ns	$9.42 * 10^{+12}$ sec ( $2.99 * 10^5$ years)
22.5 ns	$1.40 * 10^{+15}$ sec ( $4.43 * 10^7$ years)
25.0 ns	$2.07 * 10^{+17}$ sec ( $6.58 * 10^9$ years)
27.5 ns	$3.08 * 10^{+19}$ sec ( $9.76 * 10^{11}$ years)
30.0 ns	$4.57 * 10^{+21}$ sec ( $1.45 * 10^{14}$ years)
32.5 ns	$6.78 * 10^{+23}$ sec ( $2.15 * 10^{16}$ years)
35.0 ns	$1.01 * 10^{+26}$ sec ( $3.19 * 10^{18}$ years)

RTL Hardware Design  
by P. Chu

Chapter 16

36

- Observations

- MTBF is statistical average
- Only  $T_r$  can be adjusted in practical design
- MTBF is extremely sensitive to  $T_r$ 
  - Good: synchronization failure can be easily avoided by providing additional resolution time
  - Bad: minor modification can introduce synchronization failure


## 5. Synchronizer

- Synchronization circuit:

- Synchronize an asynchronous input with system clock
- No physical circuit can prevent metastability
- Synchronizer just provides enough time for the metastable condition to be “resolved”

- E.g.,

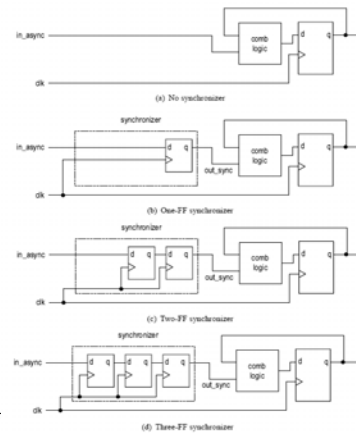- $w=0.1\text{ns}$ ,  $\tau=0.5\text{ns}$ ,  $f_{\text{clk}}=50\text{MHz}$ ,  $f_d=0.1f_{\text{clk}}$
- $T_{\text{setup}}=2.5\text{s}$



## No synchronizer

- $T_r = 0$
- $MTBF(0) = 0.04\text{ ms}$

## One-FF synchronizer

- $T_r = T_c - (T_{\text{comb}} + T_{\text{setup}})$
- $T_r$  depends on  $T_c$ ,  $T_{\text{setup}}$  and  $T_{\text{comb}}$ 
  - $T_c$ : vary with system specification
  - $T_{\text{comb}}$ : vary with circuit, synthesis (gate delay), placement & routing (wire delay)
- E.g.,
  - $T_r = 20 - (T_{\text{comb}} + 2.5) = 17.5 - T_{\text{comb}}$
  - $T_{\text{comb}} = 1\text{ns}$ ,  $T_r = 16.5\text{ns}$ ;  $MTBF(16.5) = 272\text{yr}$
  - $T_{\text{comb}} = 12.5\text{ns}$ ,  $T_r = 5\text{ns}$ ;  $MTBF(5) = 0.88\text{ns}$
- Not a reliable design

## Two-FF synchronizer

- Add an extra FF to eliminate  $T_{comb}$ 
  - $T_r = T_c - T_{setup}$
  - $T_r$  depends on  $T_c$  only
  - Async input delayed by two clock cycles
- E.g.,
  - $T_r = 20 - 2.5 = 17.5$ ; MTBF(17.5)=3000yr
- Most commonly used synchronizer
- In ASIC technology
  - May have “metastability-hardened” D FF cell (large area)

## Three-FF synchronizer


- Add an extra stage to increase resolution time
  - $T_r = 2(T_c - T_{setup})$
  - Async input delayed by three clock cycles
- E.g.,
  - $T_r = 2 \times (20 - 2.5)$ ; MTBF(30)=6 billion yr
- Hardly needed

## Observation

- $T_r$  is in the exponent of MTBF equation
- Small variation in  $T_r$  can lead to large swing in MTBF
 
## Proper use of synchronizer

- Use a glitch-free signal for synchronization
- Synchronize a signal in a single place
- Avoid synchronization multiple “related” signals.
- Reanalyze the synchronizer after each design change



## Why synchronization is a “tricky” issue

- Metastability is basically an “analog” phenomena
- Metastability behavior is described by random variable
- Metastability cannot be easily modeled or simulated in gate level (only ‘X’)
- Metastability cannot be easily observed or measured in physical circuit (e.g., MTBF = 3 months)
- MTBF is very sensitive to circuit revision



## 6. Enable tick crossing clock domain

## Signals crossing clock domains


- Synchronizer
  - Just ensures that the receiving system does not enter a metastable state
  - Not guarantee the “function” of the received signal
- Consideration
  - One signal
  - Multiple signals (“bundled data”)

## Domain-crossing of an enable signal

- An enable tick
  - One-clock-cycle wide
  - To be sample in a single clock edge
  - E.g., enable input of a counter; read/write signal of a FIFO buffer
  - Can also be used to retrieve bundled data
 
## “Wide” enable signal

- From a slow clock domain to a fast clock domain (e.g., 1 MHz to 10 MHz)




- Will this work?


 
## “Narrow” enable signal

- From a fast clock domain to a slow clock domain (e.g., 10 MHz to 1 MHz)
- The enable pulse is probably too narrow to be detected
- Need to “stretch” the pulse
  - Cannot be done by a normal sequential circuit
  - Need to use “tricks”



- en\_q asserted at the rising edge of en\_in
- en\_q then synchronized
- en\_strobe then clears stretcher
- en\_q may last over two clock cycles and thus an edge-detector is needed
- Can this scheme be used for wide-pulse?

RTL Hardware Design  
by P. Chu

Chapter 16

55


## Level-alternating scheme

- Output interface of sender and input interface of receiver modified for domain crossing
- Output interface converts an “edge-sensitive” enable pulse to a level-alternating signal
  - Use a T-FF
- Input interface converts the level-alternating signal back to “edge-sensitive” enable pulse
  - Use a dual-edge detector
- Eliminate the ad-hoc stretcher and follow the synchronous design methodology

RTL Hardware Design  
by P. Chu

Chapter 16

56

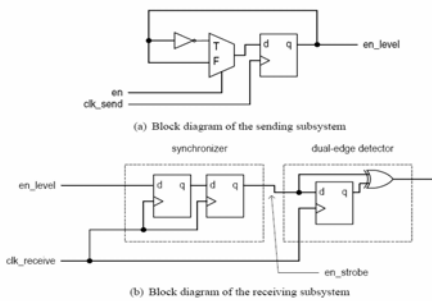

RTL  
by P

(c) Simplified timing diagram

57



## 6. Handshaking

- How to control the rate of data (or number of enable ticks) between two clock domains? (e.g., 10 MHz system to 1 MHz system)
- Does the sending system have prior knowledge about the processing speed of receiving system?
- Handshaking scheme
  - Use a feedback signal
  - Make minimal assumption about the receiving system

RTL Hardware Design  
by P. Chu

Chapter 16


59

  

RTL Hardware Design  
by P. Chu


Chapter 16

60

 


- Four phases:
  - Phase 1: talker activates req
  - Phase 2: listener activates ack
  - Phase 3: talker de-activates req
  - Phase 4: listener de-activates ack
  - Talker can start a new request

 - Need synchronizer if talker listener in different clock domains




- Talker FSM and listener FSM

 


- Implementation:
  - Talker: FSM and synchronizer for ack\_out
  - Listener: FSM and synchronizer for req\_out
- Pass an enable tick using handshaking
  - The enable tick functions as the start signal in talker
  - The listener generates a Mealy output which is asserted when req\_sync is asserted in the s\_ack0 state (i.e., a rising-edge detection circuit for req\_sync)

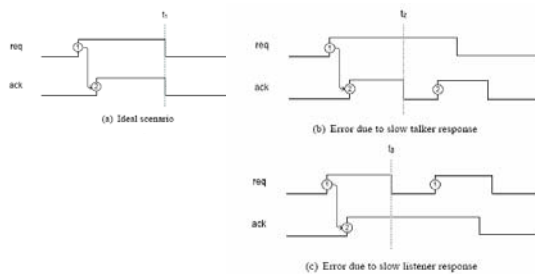- Can we remove the second part of handshaking?



 
- Two-phase handshaking protocol
  - We can modify the 4-phase protocol so that talker/listener not returning to 0
  - May not be proper for certain applications



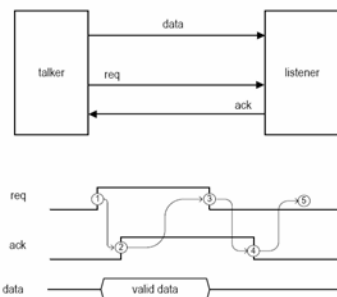
## 6. Data transfer crossing clock domains

- It is difficult to synchronize a multiple-bit signal (e.g., signal changes from 11 to 00)
- Use req/ack and handshaking protocol to coordinate data transfer
  - Only one signal needs to be synchronized in each domain
  - All other signals are bundled as “data”


- Push operation (talker sending data)
  - Conceptual diagrams



 
- More detailed diagram
  - Talker activates req\_out and tri\_en (i.e., placing data on data bus) at the same time.
  - req\_out is delayed one or two clocks when synchronized in listener
  - data is stabilized when data\_en is asserted (i.e., no timing violation)



 - Pull operation (taller retrieving data)
  - Conceptual diagrams



 - Bidirectional operation is possible; e.g.,



- Performance:
  - How many clock cycle for one data transfer?
- Other methods for data transfer
  - FIFO (synchronization needed for empty and full status signal)
  - Shared memory (synchronization needed for arbitration circuit)
  - Dual-port memory (meta-stable condition may occur in the internal arbitration circuit)