
 


Question 1

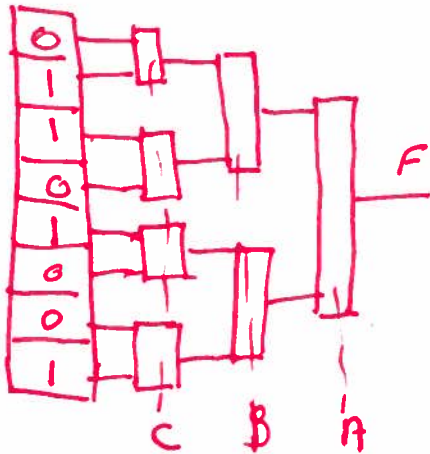a) $F(A, B, C) = \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC + \bar{A}\bar{B}C = \sum m(1, 2, 4, 7)$




COEN 6501 Final Dec 12, 2015

$$Z = 0.25XY + 1 = \frac{1}{4}XY + 1$$

First Evaluate XY then shift right by 2 places to divide by 4. Now Add the '1' to the left of the binary Point.

 
Alternatively you may multiply XY by 0.01 binary and then add the 1 before the binary Point



Area 9 Full Adders + 16 AND gate

Delay 2 Full Adder + 5 Half Adder delay + AND gate delay

Question 3

 


Present state y_2, y_1, y_0	Next state	
	$x=0$	$x=1$
0 0 0	0 0 0	1 0 0
0 0 1	0 0 0	1 0 0
0 1 0	0 0 1	1 0 1
0 1 1	0 0 1	1 0 1
1 0 0	0 1 0	1 1 0
1 0 1	0 1 0	1 1 0
1 1 0	0 1 1	1 1 1
1 1 1	0 1 1	1 1 1

From the Transition Table

$$y_2^+ = x = D_2$$

$$y_1^+ = y_2 = D_1$$

$$y_0^+ = y_1 = D_0$$

 

Question 4

- a) There are 3 paths:
- Path 1 $U_4 \rightarrow U_3 \rightarrow U_5$
 - Path 2 $U_5 \rightarrow U_2 \rightarrow U_4$
 - Path 3 $U_5 \rightarrow U_4$

- b) Evaluating the paths, path 3 can be neglected

$$\gamma = \gamma_{cq} + \gamma_{cl} + \gamma_{su}$$

For path 1 $\gamma_1 = 1.5 + 0.15(2) + 0.2 \times 2 + 0.2 + 0.05(2+1) + 0.14 \times 2 + 1 = 3.83 \text{ ns}$

Path 2 $\gamma_2 = 1.5 + 0.15(1.5+2) + 0.2 \times 2 + 0.4 + 0.12 \times 2 + 0.18 + 1 = 4.24 \text{ ns}$

So path 2 is the critical path $\gamma_{\max} = 4.245$
 $f_{\max} = 236 \text{ MHz}$

- c) For K input of FF- U_5 the path is path 1 $U_4 \rightarrow U_3 \rightarrow U_5$

$$\text{Set up time slack} = T_{\text{required}} - T_{\text{arrival}}$$

$$T_{\text{required}} = T_{\max} - T_{su} = 4.245 - 1 = 3.245 \text{ ns}$$

$$T_{\text{arrival}} = \gamma_{cq} + \gamma_{cl} = 1.5 + 0.15 \times 2 + 0.2 \times 2 + 0.2 + 0.05(2+1) + 0.14 \times 2 = 2.83 \text{ ns}$$

$$T_{\text{set up slack}} = 3.245 - 2.83 = 0.415 \text{ ns}$$

or $= 0.615$ if fan out output neglected

$$\text{hold time slack} = \gamma_{\text{arrival}} - \gamma_{\text{hold}} = 2.83 - 0.5 = 2.33$$

No Violation

or $= 2.13$
 if fan-out of output is neglected

Q5

- a) Two paths $D4-U3-D5$
 $D5-U2-D4$

$$\left. \begin{array}{l} \text{Path 1. } 2 + 0.45 * 3 + 0.4 + 0.35 * 4 = 5.15 \text{ ns} \\ \text{Path 2. } 2 + 0.45 * 1 + 0.2 + 0.15 * 4 = 3.25 \text{ ns} \end{array} \right\}$$

Arrival at Point F = Delay of D4 = $t_{CQ} + t_{CL} + \text{Fanout} = \underline{3.35}$

Required time at X = $20 \text{ ns} - t_{su} - \text{Delay of U3}$
 $= 20 - 1 \text{ ns} - 1.8 \text{ ns} = \underline{17.20 \text{ ns}}$

Slack time at F = $17.20 - 3.35 = \underline{13.85 \text{ ns}}$

- b) Path 1 is the critical path $D4-U3-D5$

$T_{i \max} = T_{CL} + T_{CL} + T_{CQ} = 5.15 + 1 = 6.15 \text{ ns}$

Temp effd, $k_t = \left(\frac{T_J - 25^\circ \text{C}}{30^\circ \text{C/W}} \right)^M = \left(\frac{273 + 70}{273 + 25} \right) = \left(\frac{343}{298} \right)^{1.5} = \underline{1.235}$

Voltage effd $k_v = \frac{1}{1 - 0.05} = \underline{1.0526}$

$K = k_t * k_v = 1.235 * 1.0526 = \underline{1.3}$

Overall Delay = $K * T_{i \max} = 1.3 * 6.15 = \underline{8 \text{ ns}}$

worst case frequency, $f = \frac{1}{8 \text{ ns}} = 125 \text{ MHz}$

Question 6 p1

Assume the following decoding

x y
 0 0
 0 1
 1 0
 1 1

$x = y$
 $y > x$
 $x > y$
 X

Then

$A_{i+1} B_{i+1} x y$	A_i	B_i
0000	0	0
0001	0	1
0010	0	0
0011	0	1
0100	0	0
0101	0	1
0110	0	0
0111	0	1
1000	1	0
1001	1	1
1010	1	0
1011	1	1
1100	1	0
1101	1	1
1110	1	0
1111	1	1

$A_{i+1} B_{i+1} x y$	00	01	11	10
00	0	0	X	1
01	0	1	X	1
11	1	1	X	1
10	1	0	X	1

$A_{i+1} B_{i+1} x y$	00	01	11	10
00	0	1	X	0
01	1	1	X	0
11	1	1	X	0
10	1	0	X	0

$$A_i = A_{i+1} + \bar{B}_{i+1} x \bar{y}$$

$$B_i = B_{i+1} + \bar{A}_{i+1} \bar{x} y$$

Now that we have the Boolean expression for A_i & B_i we can proceed and the VHDL code for the bit Comparator and the easiest would be a behavioral description.

library IEEE;

use IEEE STD_LOGIC_1164_411;

-- other use statements of STD library if needed

entity Component_1 is

Port (Ain, Bin, x, y: in std_logic; A0, B0: out std_logic);

end Component_1

architecture behavioral of Component_1 is

begin process (Ain, Bin, x, y)

begin if (Ain = '1' and Bin = '0') then A0 <= '1'; B0 <= '0';

elsif (Ain = '0' and Bin = '1') then A0 <= '0'; B0 <= '1';

elsif (x = '1' and y = '1') then A0 <= '0'; B0 <= '0';

else A0 <= x; B0 <= y;

end if;

end process;

end behavioral;

Question 6 - Continued P2

-- library statements here ..

entity component_8 is

Port (Ain, Bin : in std_logic;
x, y : in std_logic_vector 7 downto 0); Ao, Bo : out std_logic);
end component_8;

architecture structural of component_8 is

Component_1

Port (Ain, Bin, x, y : in std_logic; Ao, Bo : out std_logic);
end Component_1

signal sa, sb : std_logic_vector(7 downto 0);

begin

for comp7 : Component_1 use entity work Component_1 (behavioral);
comp7 : Component_1 Portmap (Ain, Bin, x(7), y(7), sa(7), sb(7));

for comp6-1 : Component_1 use entity work Component_1 (behavioral);
stages: for i in 6 downto 1 generate

comp6-1 : Component_1 Portmap (sa(i+1), sb(i+1), x(i), y(i), sa(i), sb(i));

end generate;

comp0 : Component_1 Portmap (sa(1), sb(1), x(0), y(0), Ao, Bo);

end structural;